

## **CE3002 - Sensors, Interfacing and Control**

### **Contents:-**

- 1-Components used
- 2-AD625 Circuit connection
- 3-Software procedures, Troubleshooting
- 4-To obtain a waveform of 500 mHz at 40mVpp from Function Generator SDG800

#### **1a) Components used :-**

##### **1) Resistors – ¼ W :-**

100K ohm – 2 pcs

1.2M ohm -1 pc

1.6K ohm – 1 pc

1K ohm – 4 pcs

**½ W, 150 ohm** – 2 pcs (size is bigger than ¼ W, Voltage divider)

##### **2) Capacitors :-**

Tantalum, polarised – 0.22 uF

Electrolytic, polarised – 10 uF

##### **3) Trimmer – 10K ohm – 1 pc (square, single-turn, 3pin)**

**Potentiometer** – 10K ohm – 1 pc ( Round Metallic, 3pin terminal )

##### **4) IC chip**

Op Amp - uA741, 8-pin – 2 pcs

Instrumentation Amp, AD625, 16-pin – 1 pc


##### **5) Plethysmograph, PPG 1020FC – 1 set ( Signal, Ground, 7.5V)**

##### **6) Arduino Uno R3 with USB cable – 1 set**


**1b) Some component cost :-**

| <b>S/N</b> | <b>Description</b>   | <b>Qty</b> | <b>Unit Price (SGD)</b> |
|------------|--|------------|-------------------------|
| 1.         | <i>Black customized Bag with Strap</i>                                   | 1          | 38.00                   |
| 2.         | <i>Project Breadboard GL 36</i>  | 1          | 34.00                   |
| 3.         | <i>Goot YS-2 Wire stripper cum cutter</i>                                | 1          | 18.90                   |
| 4.         | <i>Goot YPS-2 long nose plier</i>  | 1          | 16.00                   |
| 5.         | <i>IC Extractor</i>  | 1          | 5.00                    |
| 6.         | <i>Screw driver (-)</i>  | 1          | 2.50                    |
| 7.         | <i>Power Supply cable, Pair</i>  | 2          | 10.00                   |
| 8.         | <i>Plethysmograph 1020 FC (ver 1 or 2)</i>                               | 1          | 483.00                  |
| 9.         | <i>Arduino UnoR3 board with USB cable (A to B)</i>                       | 1          | 30.00                   |
| 10.        | <i>LM741 8pin DIL ic chip</i>  | 2          | 2.80                    |
| 11.        | <i>AD625JNZ, 16 pin DIL ic chip</i>                                      | 1          | 37.35                   |
| 12.        | <i>Bag of components (resistors, capacitors, trimmer, Potentiometer)</i> | 1lot       | 15.00                   |
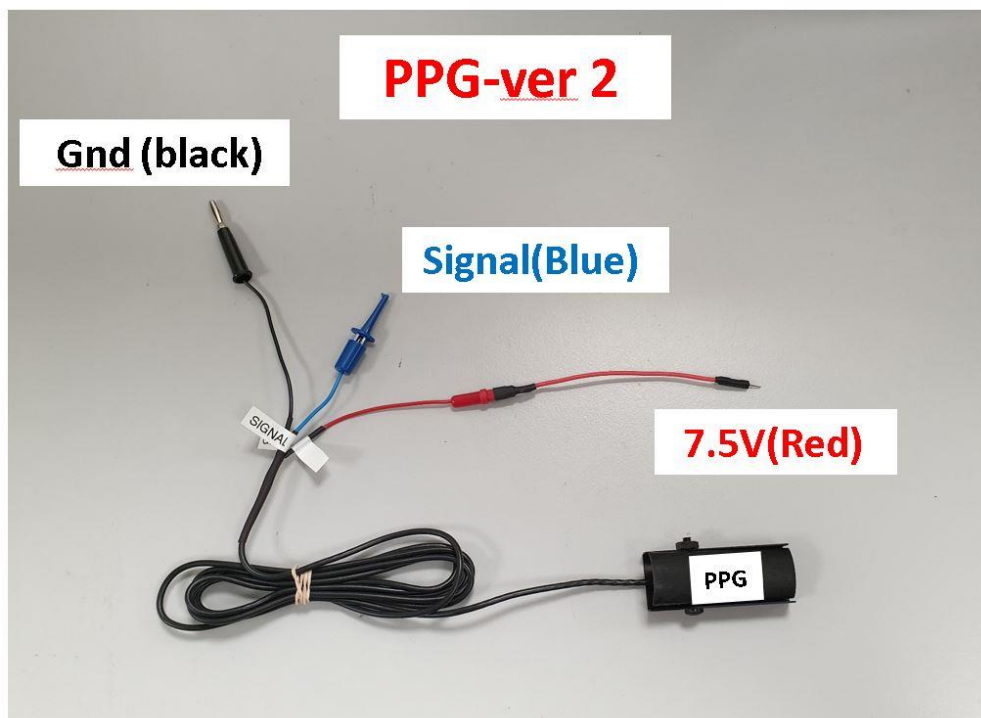
### **1c) Pulse Plethysmograph Model 1020FC**




## **2. AD625 Circuit connection**

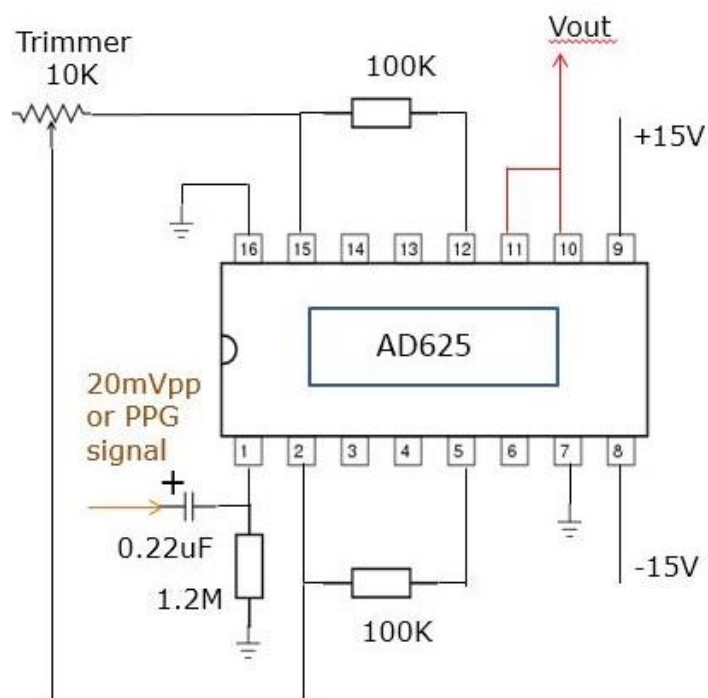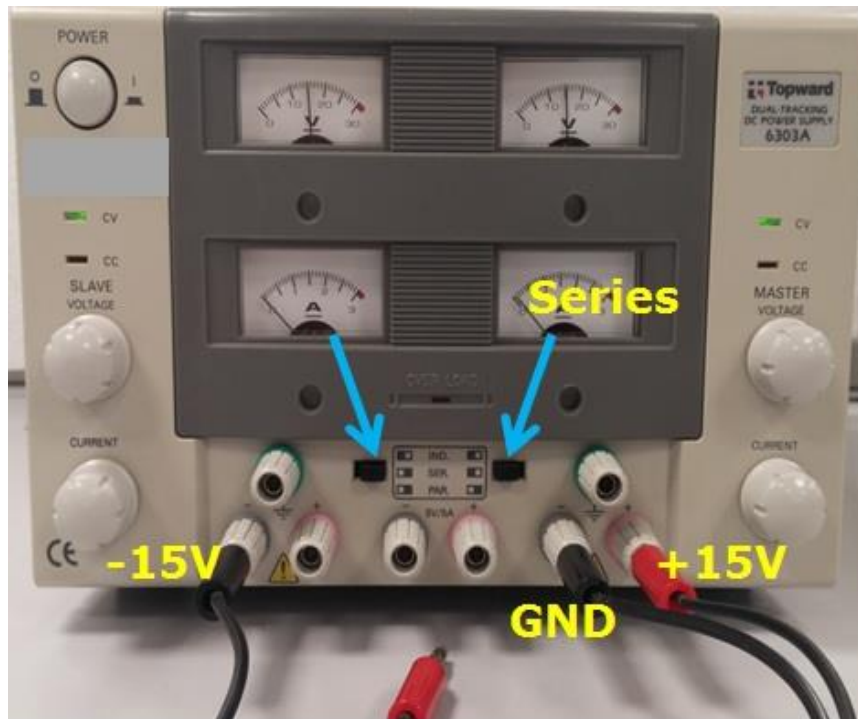




**Fig 1: AD 625 circuit**


**\*\*Note: You do not have to connect all 3 legs of the trimmer 10 K ohm, just left or right leg and the center leg.**

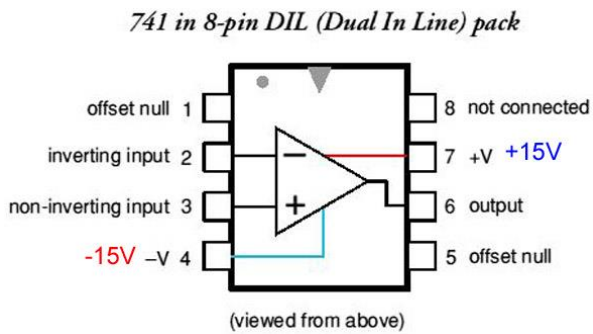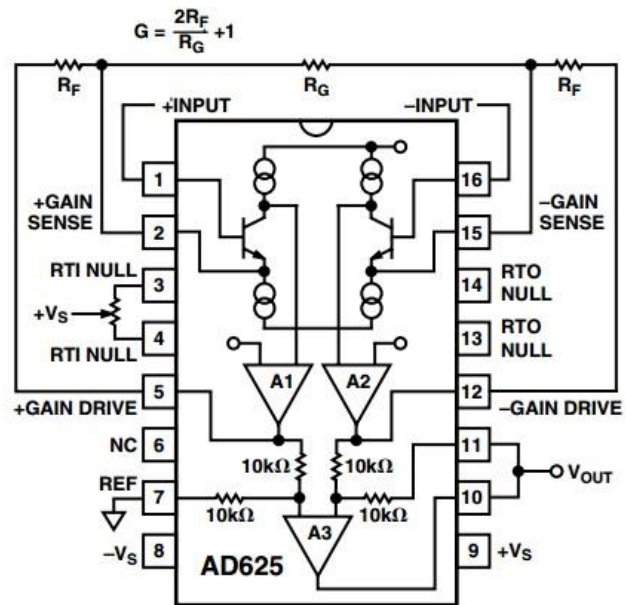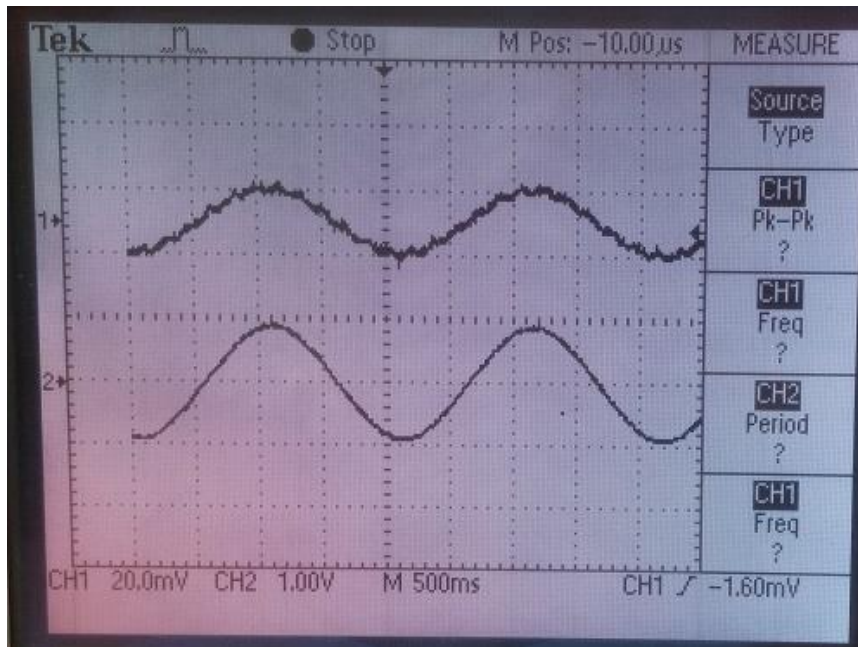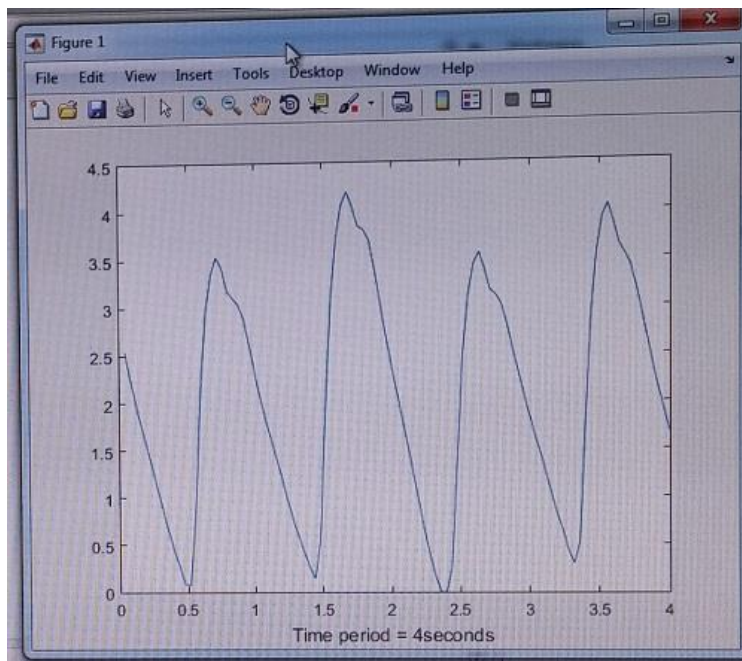**0.22uF tantalum capacitor has polarity, +ve terminal is indicated.**

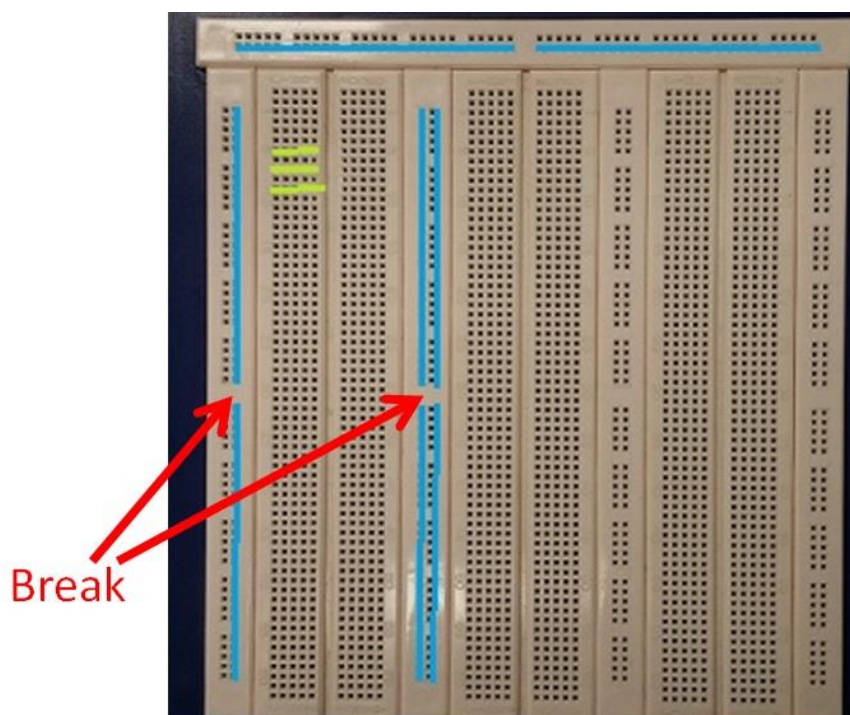


**Fig 2. Power Supply Connection**

**Fig 3a. Op amp 741 pins layout****Fig. 3b AD625 IC chip****Fig 4a. Simulated output viewed in Oscilloscope**



**Fig 4b. Waveform displayed on Matlab program (from Arduino, Offset adjusted)**



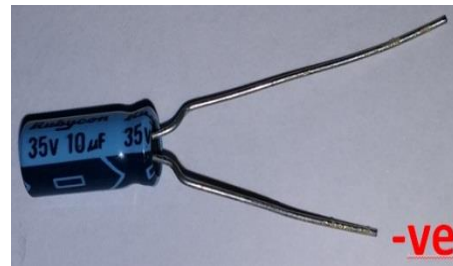
**Fig 5a. Connections in the breadboard**



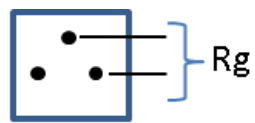
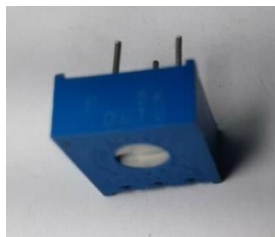
**Fig 5b. Internal pins of breadboard**



**Fig.6 Tantalum capacitor(0.22uF)**


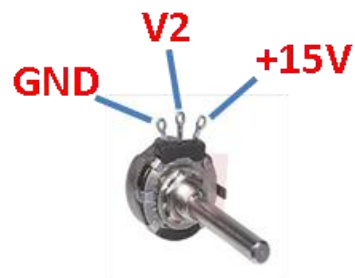


**Fig. 7 Electrolytic Capacitor (10uF)**

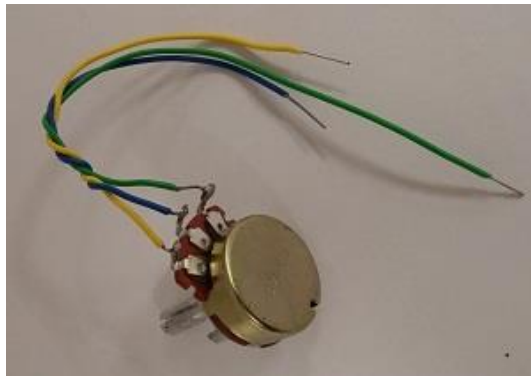

Back view of Trimmer


**Fig. 8 Trimmer (10K ohm) and connections**



Potentiometer

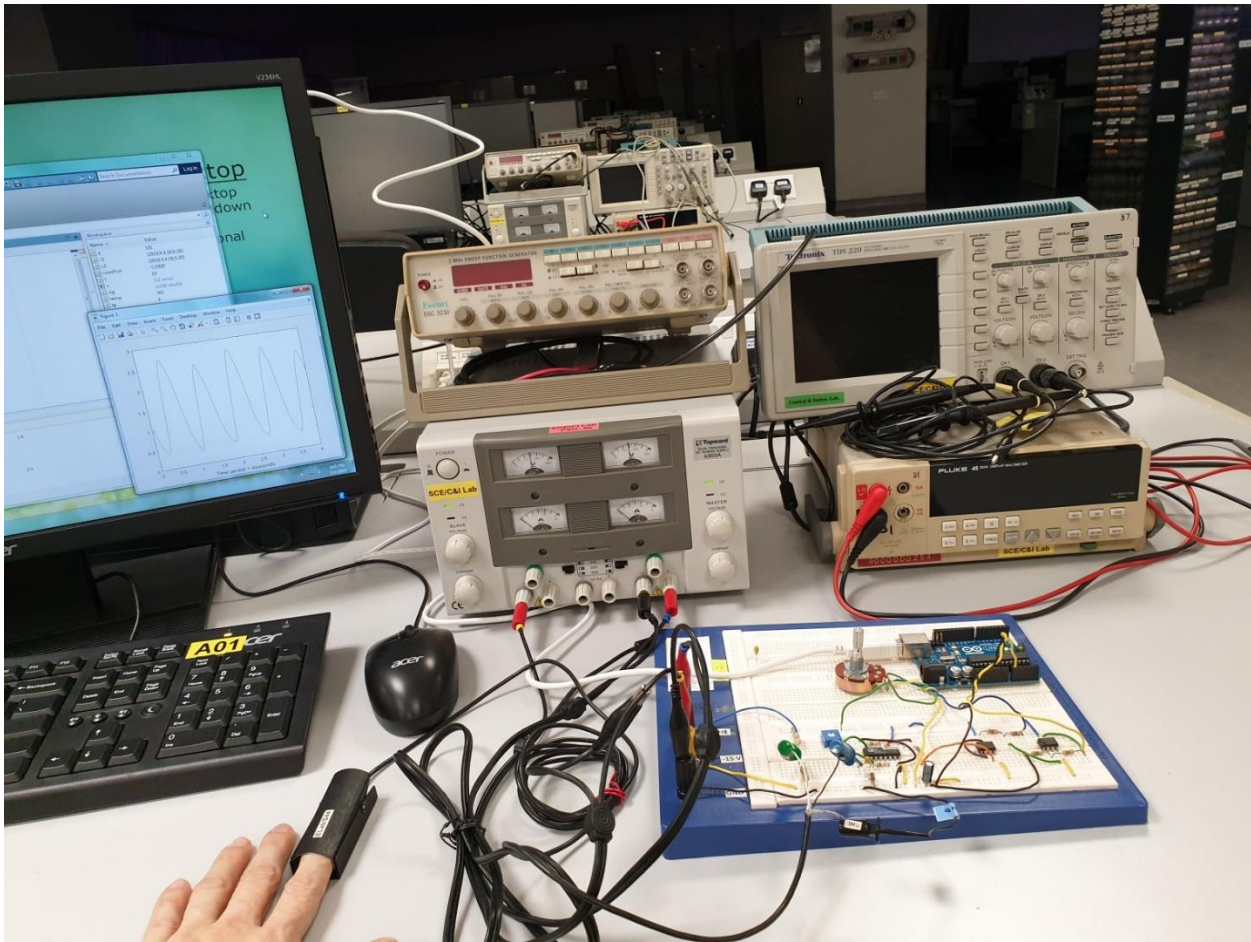**Fig. 9 Potentiometer and connections**

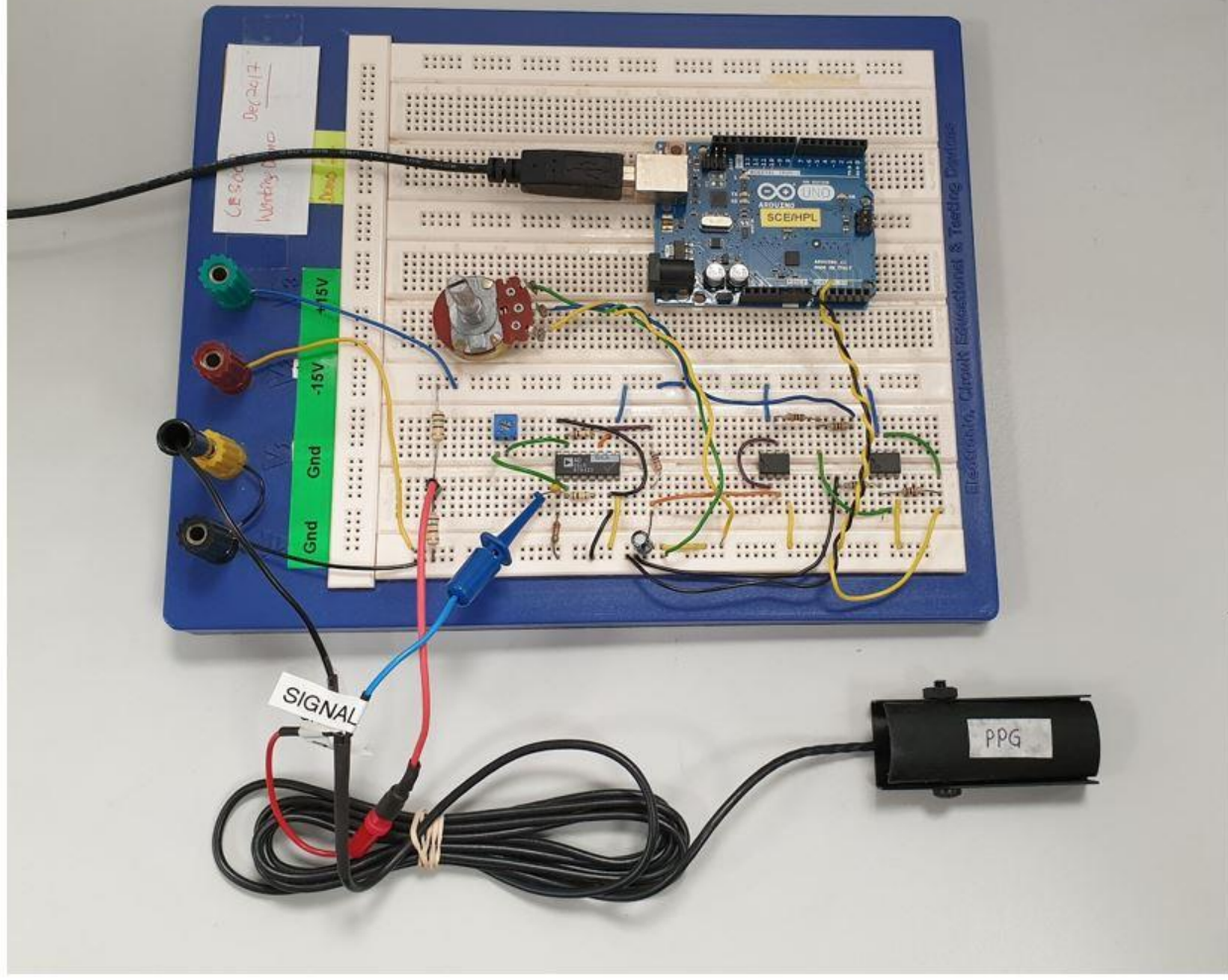




**Fig.10 Completed circuit and Screen capture of the signal**



# Breadboard connections



**Fig.10-b Completed circuit with PPG-Ver2**

### **3. Software procedures**

#### **Arduino Uno R3**

- 1) Open program in Arduino environment
- 2) Load program Analog1.ino
- 3) Let Arduino board detect the serial com port
- 4) Check serial com port number
- 5) Click 'Compile'
- 6) Click 'Verify'
- 7) Connect A0 and Gnd to Plethysmograph(PPG) circuit

#### **Matlab with Arduino addon(in HW3 and HPL labs only)**

- 1) Run Matlab2019b
- 2) Load the analog.m
- 3) Edit : comPort='Com5'; to the correct value of 5 or others
- 4) Place finger in PPG 1020FC
- 5) Click 'Run'
- 6) Wait a few seconds for graph to appear


#### **Troubleshoot the PPG 1012FC circuit**

- 1) Check voltage supplies to AD625 pin8(-15V) and pin9(+15V),  
IC741 pin4(-15V) and pin7(+15V)
- 2) Estimate 2.02k ohm for Rg
- 3) Negative terminal of 0.22uF connected to pin1 of AD625
- 4) AD625 pin16 shorted to pin7
- 5) If signal output is about 2V then circuit wiring and components are working well.
- 6) For signal with Finger in PPG 1020FC –


- a) Let power in the circuit warm up by 5 minutes.
- b) Ensure AD625 circuit has short wiring
- c) AD625 pins 7 and 16 shorted
- d) Change 0.22uF to 1 uF if the PPG signal is too weak

----- END -----
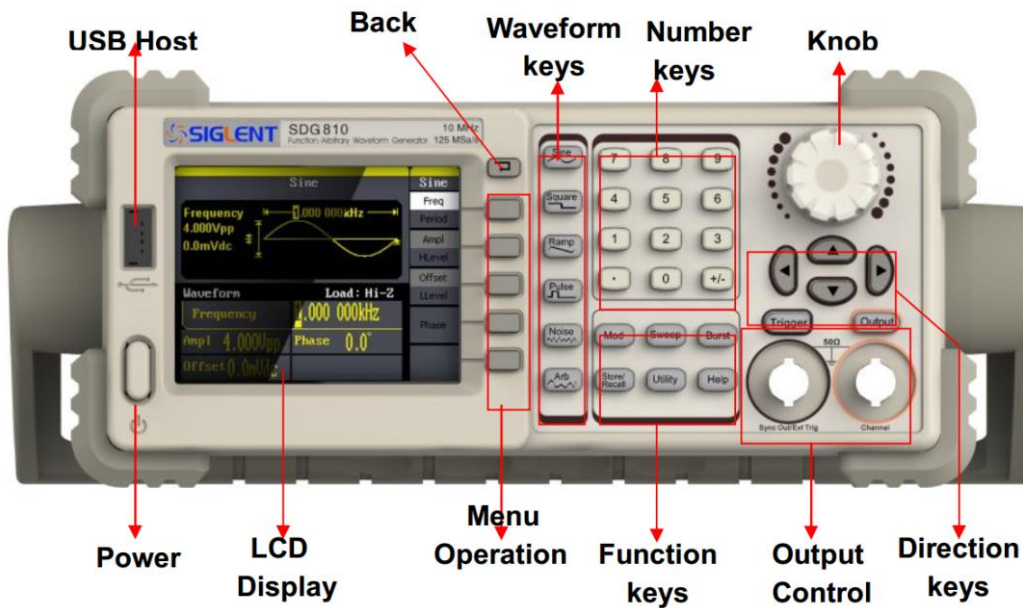
#### 4. To obtain a waveform of 500 mHz at 40mVpp from Function Generator SDG800



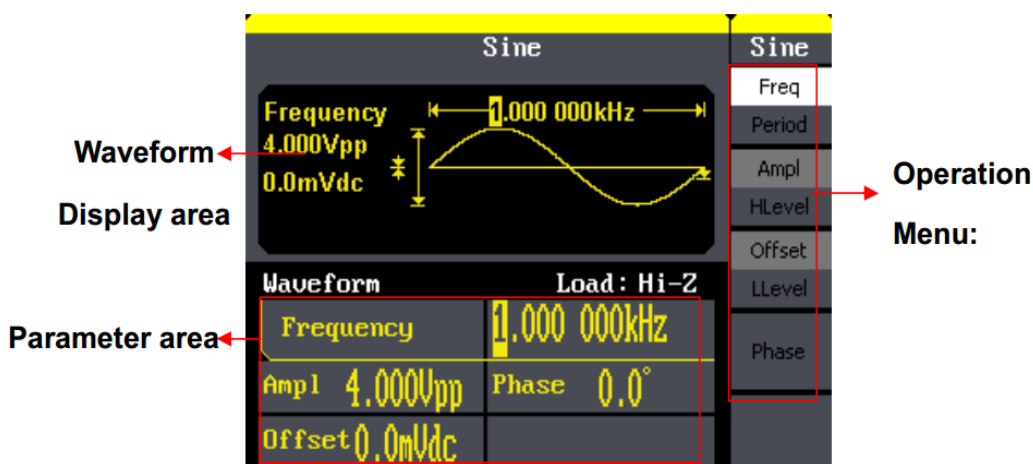- 1) Press "Sine" button.
- 2) Press "Freq" button in Menu Operation (lighted up means selected).
- 3) Key in ".5" on the Number Keys and "Hz" (i.e. 0.5 Hz).
- 4) Select "Ampl" button.
- 5) Key in "40" and select "mVpp" (40mVpp signal).
- 6) Press "Offset" to 0.00mVdc.
- 7) Leave Phase to 0.0 deg.
- 8) Waveform of Sine wave 0.5 Hz at 40mVpp is achieved.
- 9) Press "Output" button to see a signal on the Oscilloscope [Connect to oscilloscope and select Chan1=20.0mV (Volts/Div scale), and time scale to 500ms(sec/Div) ].



Output waveform of 0.5Hz, 20mVpp